
 


🔗 main ▾

...

 Digital-electronics-1 / LAB_05 / README.md



Raw

Blame



128 lines (116 sloc) | 3.96 KB

🔗 BPC-DE1 Lab_05


📎 Repository: [Bobik77](#) / [Digital-electronic-1](#) / [LAB5](#)

🔗 1. Preparation tasks:

🔗 1.1. Push-buttons connection

Push buttons are:

- HIGH when pushed
- LOW when unpushed

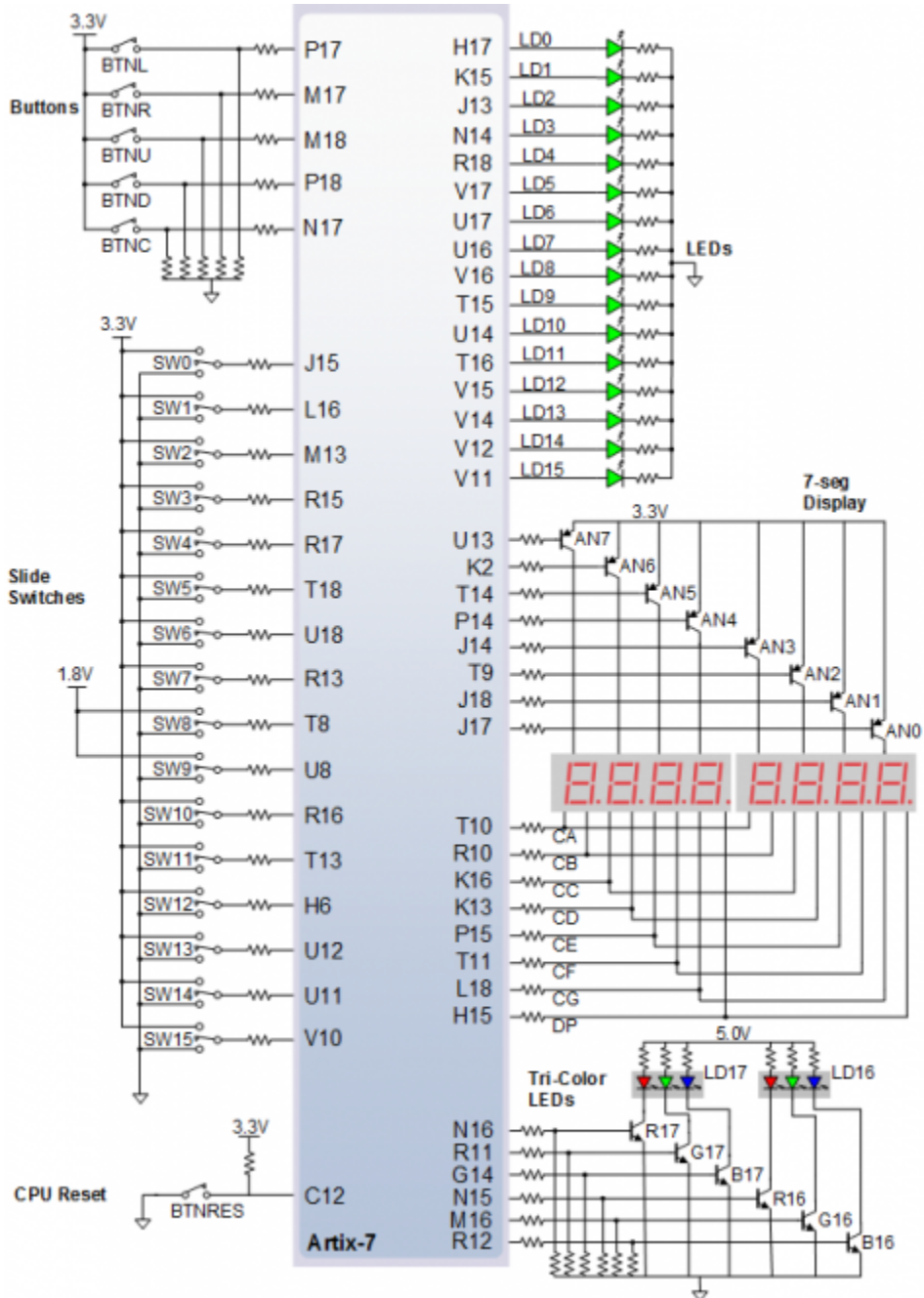

[Image source](#)

1.2. Timing table

Time interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
2 ms	200 000	x"3_0D40"	b"0011_0000_1101_0100_0000"
4 ms	400 000	x"6_1A80"	b"0110_001_1010_1000_0000"
10 ms	1 000 000	x"F_4240"	b"1111_0100_0010_0100_0000"

Time interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
250 ms	25 000 000	x"17D_7840"	b"0001_0111_1101_0111_1000_0100_0000"
500 ms	50 000 000	x"2FA_F080"	b"0010_1111_1010_1111_0000_1000_0000"
1 sec	100 000 000	x"5F5_E100"	b"0101_1111_0101_1110_0001_0000_0000"

2. Bidirectional counter

2.1. Listing of VHDL process

```
p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then                -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then              -- Test if counter is enabled
            -- Direction checking here
            if (cnt_up_i = '1') then
                s_cnt_local <= s_cnt_local + 1;
            elsif (cnt_up_i = '0') then
                s_cnt_local <= s_cnt_local - 1;
            end if;
        end if;
    end if;
end process p_cnt_up_down;
```

2.2. Listing of VHDL testbench process

```
p_reset_gen : process
begin
    s_reset <= '0';
    wait for 5 ns;
    -- Reset activated
    s_reset <= '1';
    wait for 45 ns;
    s_reset <= '0';
    wait;
end process p_reset_gen;
```

```

-- Data generation process
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;


    -- Enable counting
    s_en      <= '1';
    -- Change counter direction
    s_cnt_up <= '1';
    wait for 360 ns;
    s_cnt_up <= '0';
    wait for 220 ns;

    -- Disable counting
    s_en      <= '0';

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```

2.3. Screenshot

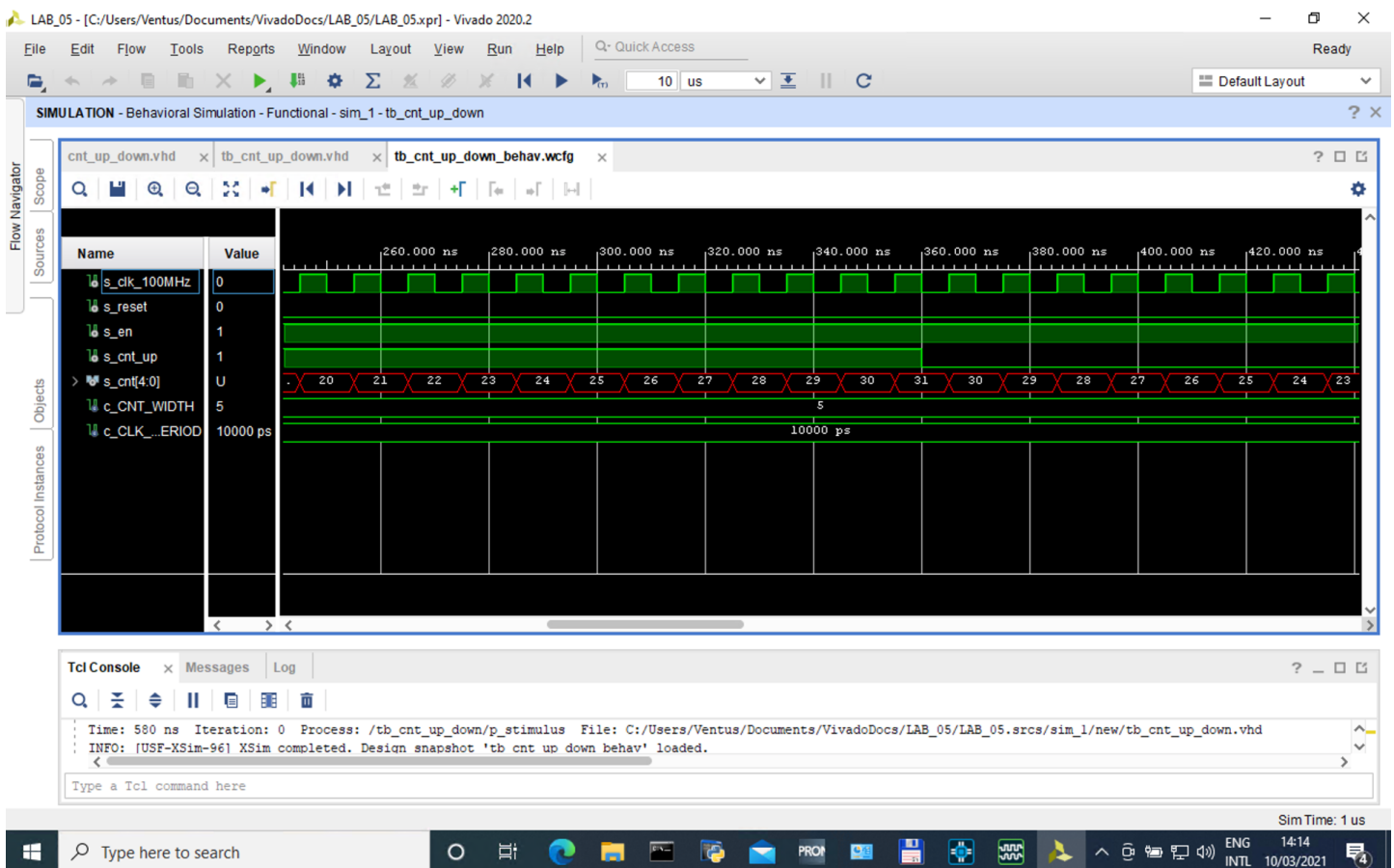

3. Top level

3.1. VHDL instances listing

```
-----  
-- Instance (copy) of clock_enable entity  
clk_en0 : entity work.clock_enable  
    generic map( g_MAX => 1000000 )  
    port map(  
        clk => CLK100MHZ,  
        reset => BTNC,  
        ce_o => s_en  
    );
```

```
-----  
-- Instance (copy) of cnt_up_down entity  
bin_cnt0 : entity work.cnt_up_down  
    generic map(g_CNT_WIDTH => 4)  
    port map(  
        clk => CLK100MHZ,  
        reset => BTNC,  
        en_i => s_en,  
        cnt_up_i => SW,  
        cnt_o => s_cnt  
    );
```

```
-- Display input value on LEDs  
LED(3 downto 0) <= s_cnt;
```

```
-----  
-- Instance (copy) of hex_7seg entity  
hex2seg : entity work.hex_7seg  
    port map(  
        hex_i    => s_cnt,  
        seg_o(6) => CA,  
        seg_o(5) => CB,  
        seg_o(4) => CC,  
        seg_o(3) => CD,  
        seg_o(2) => CE,  
        seg_o(1) => CF,  
        seg_o(0) => CG  
    );
```

3.2. Sketch of top layer with two counters

top1

