

🔗 main ▾

...

## Digital-electronics-1 / README.md

👤 Bobik77 Function table add

🕒 History

👤 1 contributor

Raw

Blame



117 lines (111 sloc) | 3.07 KB

# 🔗 Digital-electronics-1

**Name:** Vaněk Pavel, **ID:** 221072,

## 🔗 Emphasis example:

**bold**, *italic*, ***bold/italic***,

## 🔗 Lists examples:

### 🔗 Ordered

1. Základy digitálních obvodů a kombinační logiky
2. Principy sekvenčních obvodů a konečných automatů
3. Psaní kódu ve VHDL
4. Navrhování testbench ve VHDL
5. Navrhování obvodů pro FPGA

### 🔗 Unordered

- DE1
  - Bool algebra
  - VHDL
  - ...
- AE1
- AUD

## 🔗 Link example:

---

[This repository](#) was made for usage of Lecture BPC-DE1; BUT 2021.

## 🔗 Table example

---

Col1	Col2
Row2	Row2
Row3	Row3
Row4	Row4

## 🔗 Code example in VHDL:

---

```
signal input_stream : input; signal clk :std_logic; signal parity :bit ;
begin
U1: Parity_Generator1 port map(
input_stream, clk,
input1 : process (clk)
parity => parity );
begin
if clk <= 'U' then clk <= '0' after 1 ns; else clk <= not clk after 1 ns;
end if;
end process;
```

## 🔗 Programming:

---

## 🔗 De Morgan's law verification

---

## 🔗 Code of architecture

architecture dataflow of gates is

begin

-- original function:

fo\_o <= ((not b\_i) and a\_i) or ((not c\_i) and (not b\_i));

-- modified function with NORs only:


fnor\_o <= ((b\_i nor (a\_i nor a\_i)) nor (c\_i nor b\_i)) nor ((b\_i nor (a\_i nor

-- modified function with NANDs only:

fnand\_o <= ((b\_i nand b\_i) nand a\_i) nand ((c\_i nand c\_i) nand (b\_i nand b\_i

end architecture dataflow;

## Waveforms

 

## Playground link

Here is link my playground link to my play [playground program site](https://www.edaplayground.com/x/A8MC).

(<https://www.edaplayground.com/x/A8MC>)

## Function table

c	b	a	f(c,b,a)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

## Distributive laws verification 1

## Code of architecture


```

architecture dataflow of gates is
begin
    a_o <= x_i and (not x_i);
    b_o <= x_i or (not x_i);
    c_o <= x_i or x_i or x_i;
    d_o <= x_i and x_i and x_i;

end architecture dataflow;

```

## 🔗 Waveforms

 

## 🔗 Playground link

Here is link my playground link to my play [playground program site](https://www.edaplayground.com/x/jLYU).  
[\(https://www.edaplayground.com/x/jLYU\)](https://www.edaplayground.com/x/jLYU)

## 🔗 Distributive laws verification 2

### 🔗 Code of architecture

```


architecture dataflow of gates is
begin
    -- Equation A
    -- left side:
    aL_o    <= (x_i and y_i) or (x_i and z_i);
    -- right side:
    aR_o    <= x_i and (y_i or z_i);

    -- Equation B
    -- left side:
    bL_o    <= (x_i or y_i) and (x_i or z_i);
    -- right side:
    bR_o    <= x_i or (y_i and z_i);

end architecture dataflow;

```

## 🔗 Waveforms

 

Je zřejmé že rovnice platí. Provedli jsme jednoduchou zkoušku - pravá strana se rovná levé.

## 🔗 Playground link

Here is link my playground link to my play [playground program site](https://www.edaplayground.com/x/m_y5).  
([https://www.edaplayground.com/x/m\\_y5](https://www.edaplayground.com/x/m_y5))