


🔗 main ▾

⋮

Digital-electronics-1 / LAB\_03 / README.MD

 **Bobik77** Update README.MD 🕒 History

👤 1 contributor

RawBlame

✎🗑

155 lines (151 sloc) | 4.56 KB

🔗 **BPC-DE1 Lab\_03**


📎 Repository: [Bobik77 / Digital-electronic-1 / LAB3](#)

🔗 **Preparation tasks:**

🔗 **Download and install Vivado**

Done ✓

🔗 **SW and LEDs connect table:**

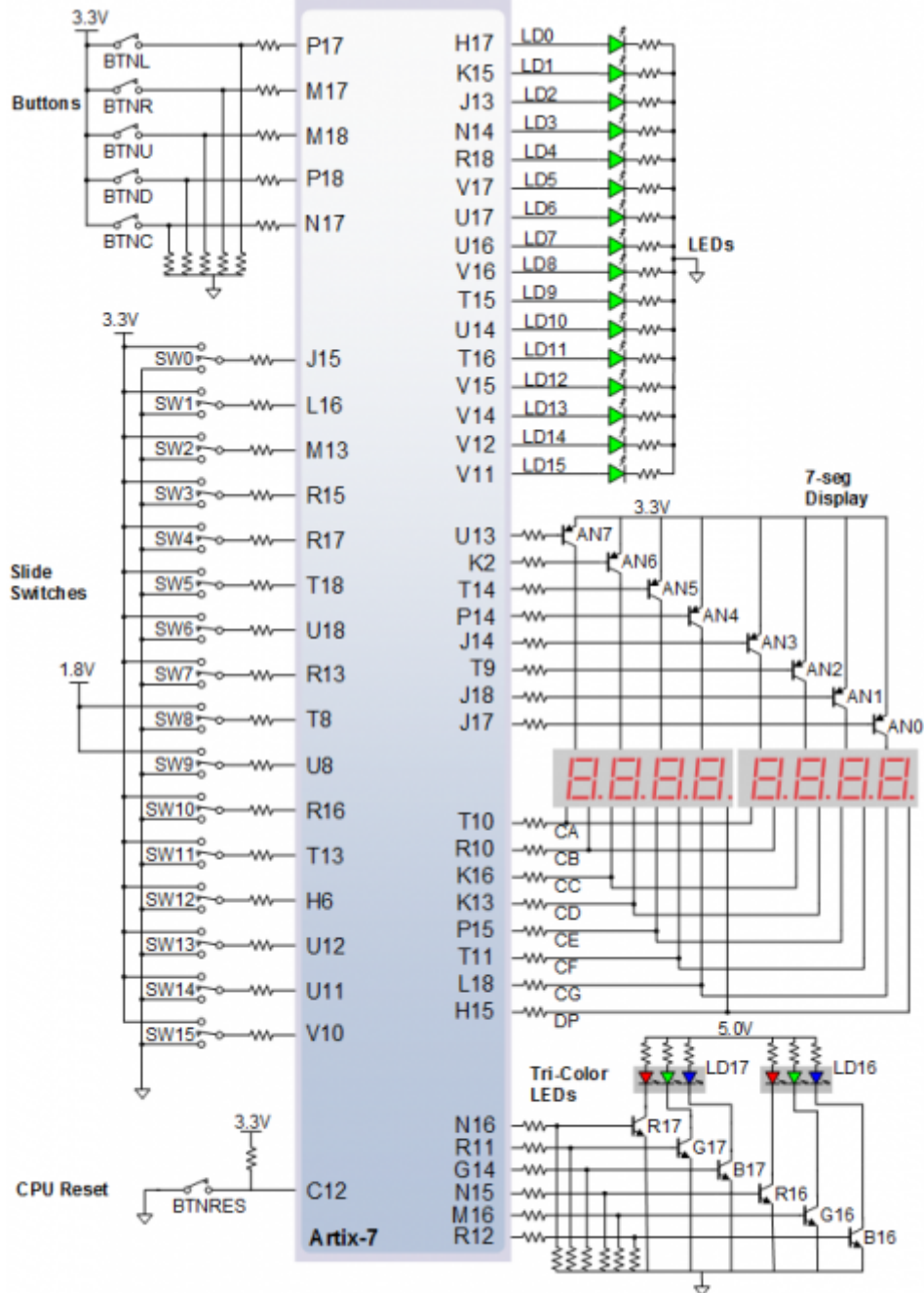

[Image source](#)

Part	PIN
LED0	H17
LED1	K15
LED2	J13
LED3	N14
LED4	R18
LED5	V17

Part	PIN
LED6	U17
LED7	U16
LED8	V16
LED9	T15
LED10	U14
LED11	T16
LED12	V15
LED13	V14
LED14	V12
LED15	V11
SW0	J15
SW1	L16
SW2	M13
SW3	R15
SW4	R17
SW5	T18
SW6	U18
SW7	R13
SW8	T8
SW9	U8
SW10	R16
SW11	T13
SW12	H6
SW13	U12
SW14	U11
SW15	V10

## 🔗 Listing architecture

```
architecture Behavioral of mux_2bit_4to1 is
begin

    process (a_i, b_i, c_i, d_i, s_i)
    begin
        case s_i is
            when "00" => q_o <= a_i;
            when "01" => q_o <= b_i;
            when "10" => q_o <= c_i;
            when "11" => q_o <= d_i;
            when others => null;
        end case;
    end process;

end Behavioral;
```

## 🔗 Listing testbench architecture


```
architecture testbench of tb_mux_2bit_4to1 is
    signal s_a      : std_logic_vector(1 downto 0);
    signal s_b      : std_logic_vector(1 downto 0);
    signal s_c      : std_logic_vector(1 downto 0);
    signal s_d      : std_logic_vector(1 downto 0);
    signal s_s      : std_logic_vector(1 downto 0);
    signal s_q      : std_logic_vector(1 downto 0);
begin
    --connecting testbench
    uut_mux_2bit_4to1 : entity work.mux_2bit_4to1
        port map(
            a_i      => s_a,
            b_i      => s_b,
            c_i      => s_c,
            d_i      => s_d,
            s_i      => s_s,
            q_o      => s_q
        );
    --Test signal generating
    p_stimuls : process
    begin
        --init. signal
        s_a <= "11";
        s_b <= "11";
        s_c <= "11";
        s_d <= "11";
        --1.st combination
        s_s <= "00";
        s_a <= "01";
        wait for 100 ns;
```

```

        s_a <= "10";
        wait for 100 ns;
        s_a <= "11";
--2.nd combination
        s_s <= "01";
        s_b <= "01";
        wait for 100 ns;
        s_b <= "10";
        wait for 100 ns;
        s_b <= "11";
--3.rd combination
        s_s <= "10";
        s_c <= "01";
        wait for 100 ns;
        s_c <= "10";
        wait for 100 ns;
        s_c <= "11";
--4.th combination
        s_s <= "11";
        s_d <= "01";
        wait for 100 ns;
        s_d <= "10";
        wait for 100 ns;
        wait;
    end process p_stimuls;
end architecture testbench;

```

## [Screenshot](#)

 


Vstupní signály byly voleny tak, aby funkčnost multiplexoru byla zjevná.


## [Vivado tutorial](#)
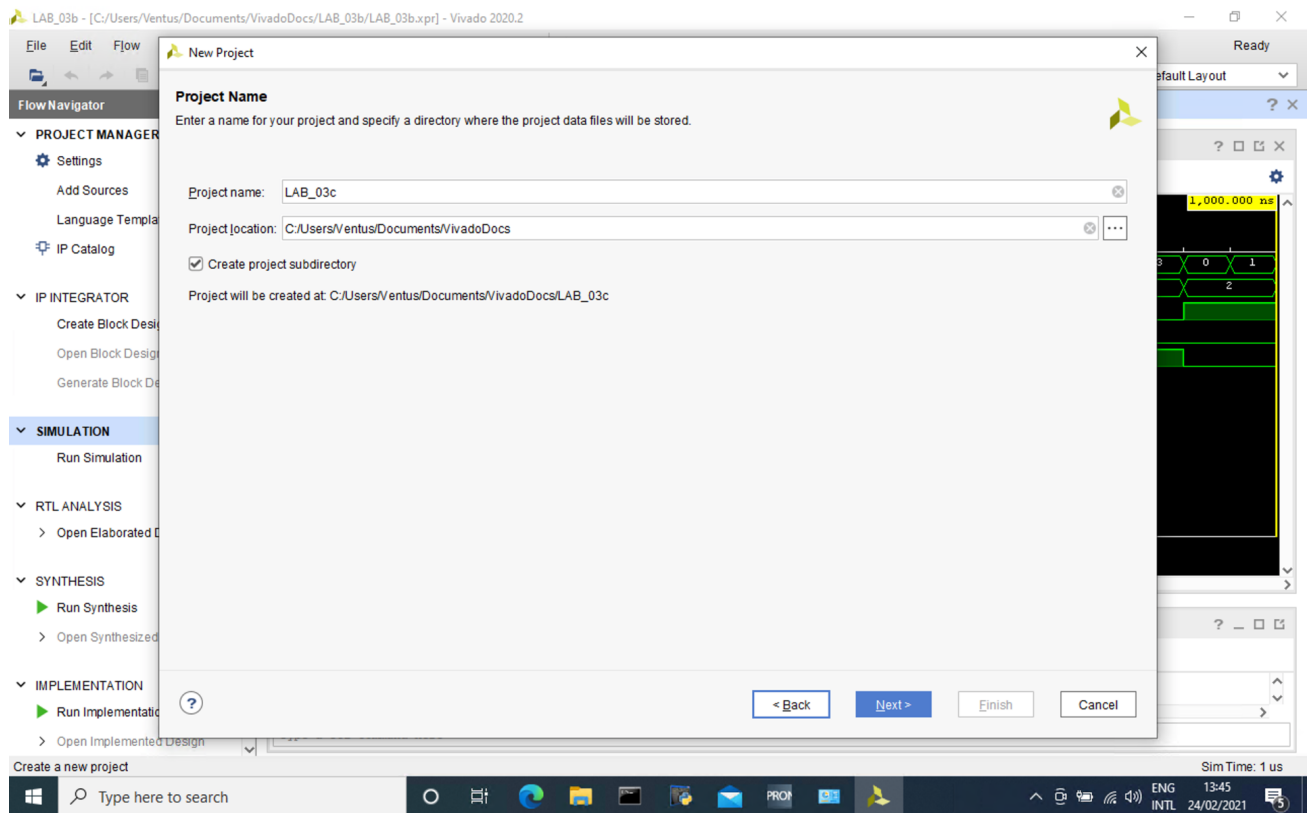
### [Project creation:](#)

- Zadej cestu projektu a vyper RTI jako typ projektu


- Vytvoř soubor (*Create file*) a pojmenuj ho. Tím se vytvoří *name.vhd* soubor kódu.



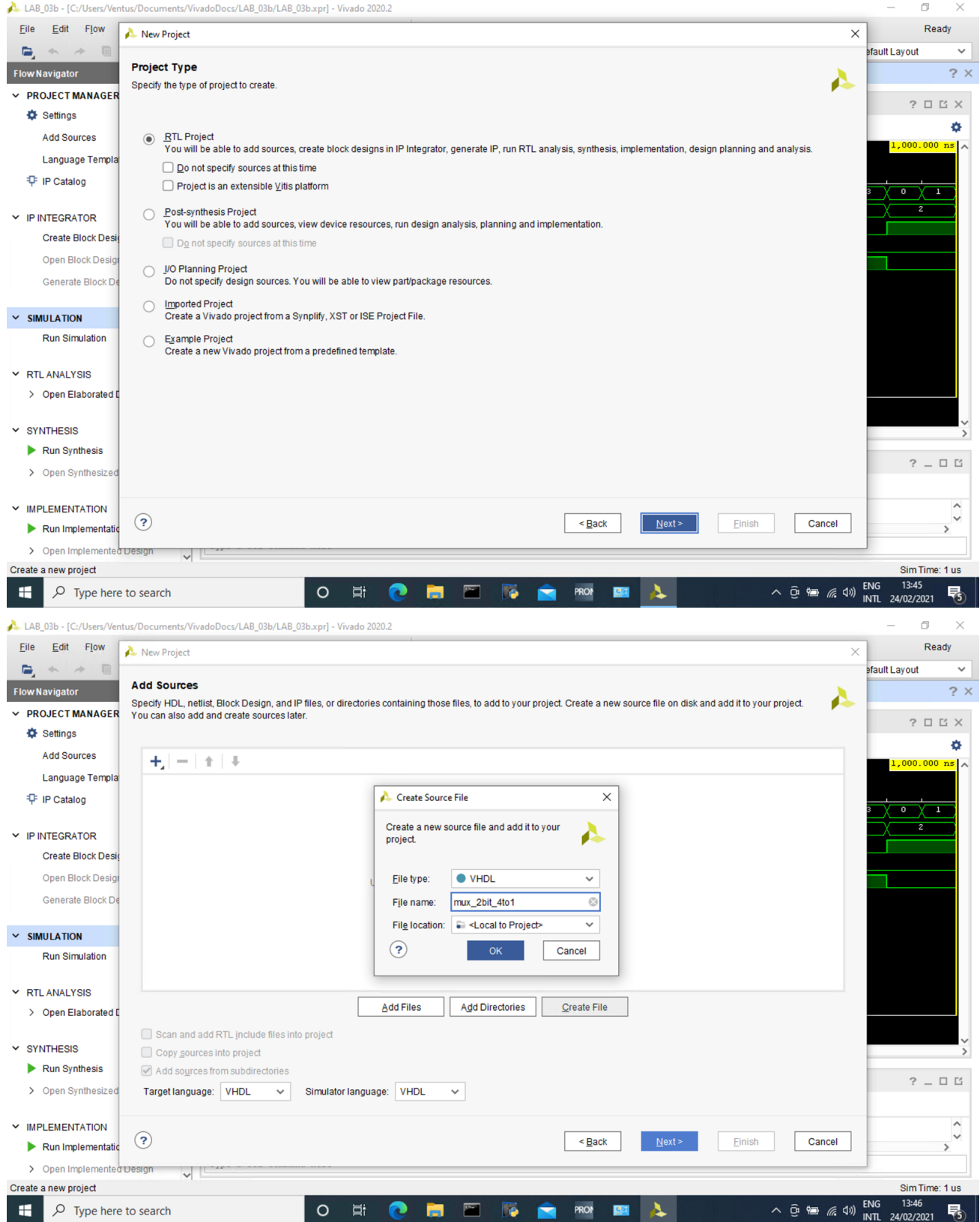
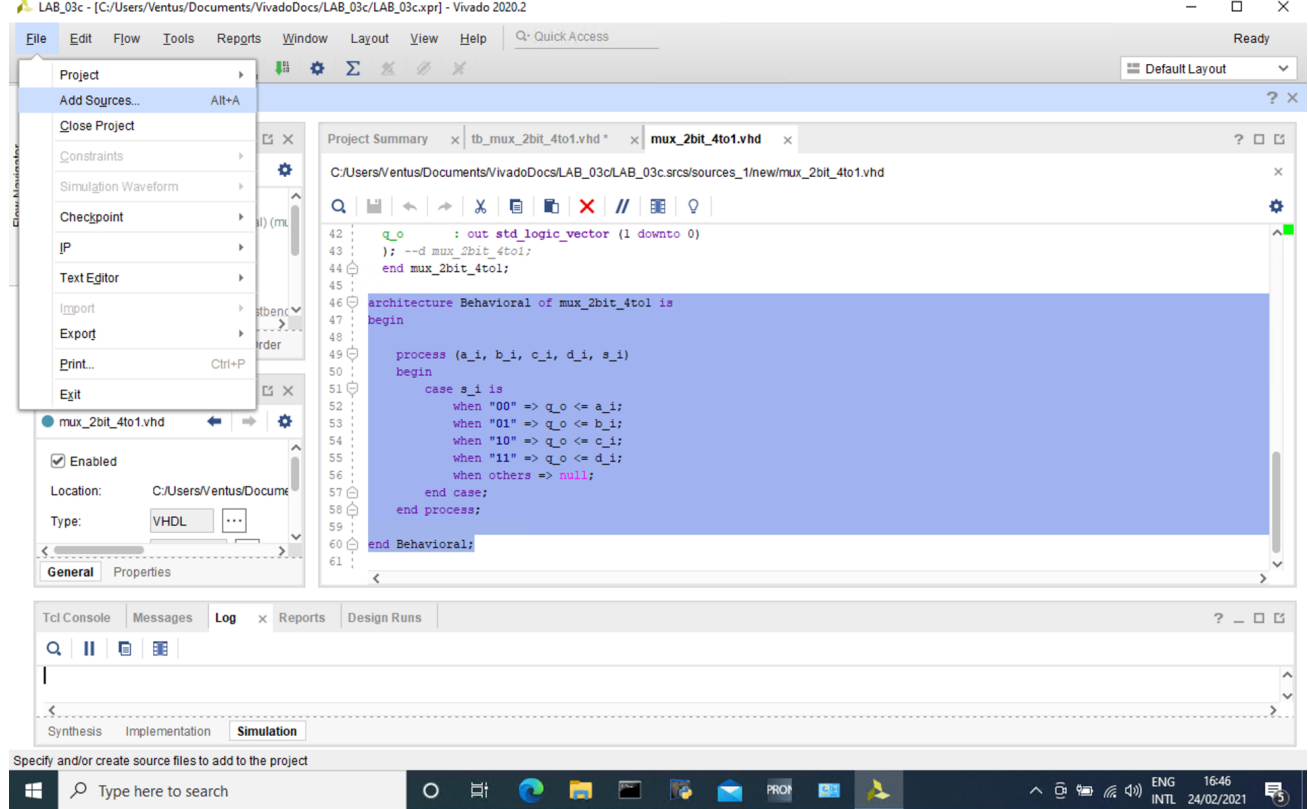
## 🔗 Testbench:

- **File > Add Sources > Add or create simulation > Create file** vytvoříme *name.vhd* soubor testbenche. Zpravidla volíme název jako *tb\_name.vhd*



- Testbench vytvoříš běžným postupem jak ses naučil např. na EDA-Playground.

## 🔗 Simulace:


- Zvolením **Flow > Run Simulation > Run Behavioral Simulation** spustíme simulaci (projekt je prvně třeba uložit).
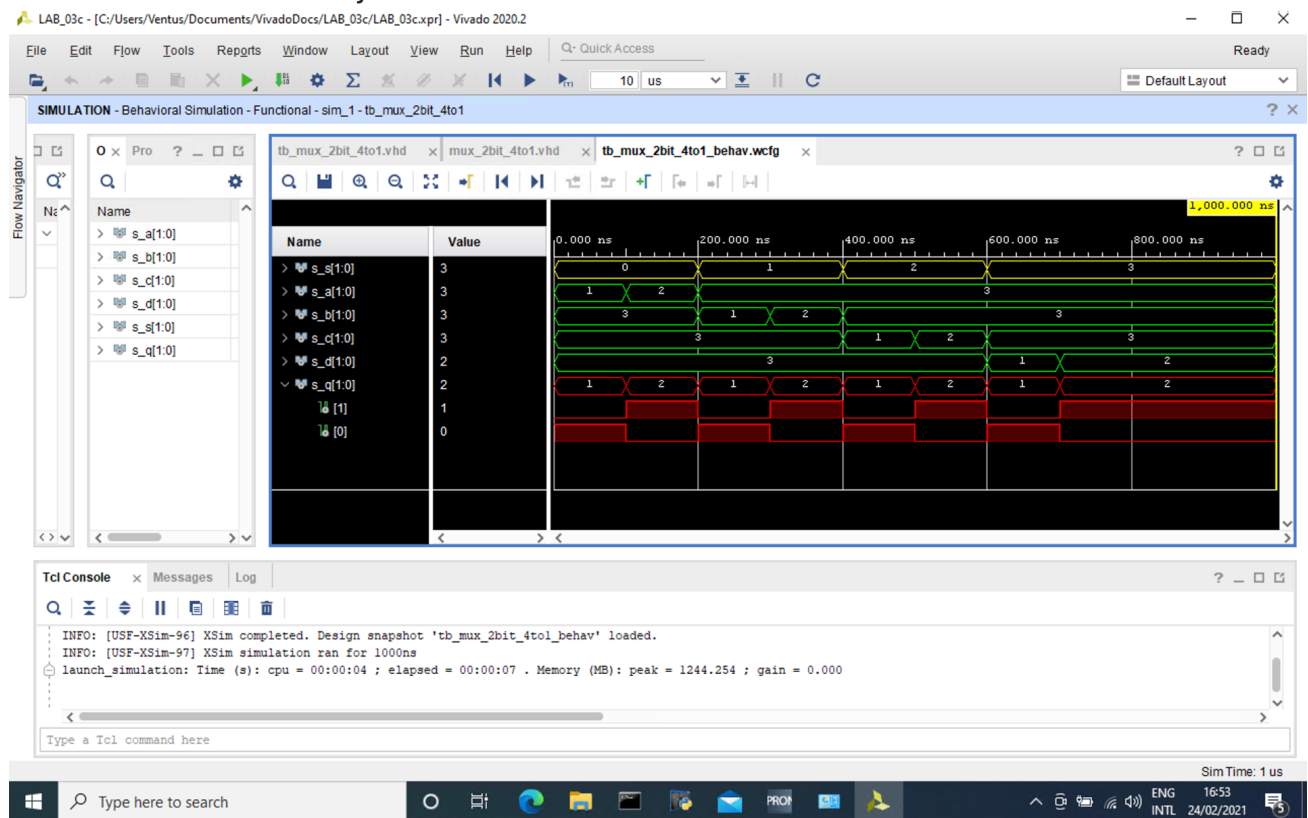
## 🔗 Postprocesor:

- V postprocesoru vidíme průběhy jednotlivých signálů
- Zvětšíme náhled na průběhy a zazoomujeme podle potřeby
- Jednotlivé sběrnice můžeme rozkliknout na signály, můžeme je libovolně podbarvovat, měřit a vizualizovat



- V nastavení simulace je možné zvětšit délku trvání simulace



## Mapování vstupů:

- **File > Add Sources > Add or create constraints > Create file** vytvoříme *name.xdc* soubor mapování.
- Do souboru mapování vložíme z předdefinovaného [souboru od výrobce](#)
- Odkomentuji ty prvky, které hodlám v programu použít
- Přepíši dané porty, tak aby odpovídali již napsané architektuře

